

CHAPTER 16 (Odd)

1. a.
$$\begin{aligned} Z_T &= j6 \Omega + 8 \Omega \angle -90^\circ \parallel 12 \Omega \angle -90^\circ \\ &= j6 \Omega + \frac{(8 \Omega \angle -90^\circ)(12 \Omega \angle -90^\circ)}{-j8\Omega - j12\Omega} = j6 \Omega + \frac{96 \Omega \angle -180^\circ}{20 \angle -90^\circ} \\ &= j6 \Omega + 4.8 \Omega \angle -90^\circ = j6 \Omega - j4.8 \Omega \\ Z_T &= j1.2 \Omega = 1.2 \Omega \angle 90^\circ \end{aligned}$$
- b.
$$I = \frac{E}{Z_T} = \frac{12 \text{ V} \angle 0^\circ}{1.2 \Omega \angle 90^\circ} = 10 \text{ A} \angle -90^\circ$$
- c.
$$I_1 = I = 10 \text{ A} \angle -90^\circ$$
- d. (CDR)
$$\begin{aligned} I_2 &= \frac{(12 \Omega \angle -90^\circ)(10 \text{ A} \angle -90^\circ)}{-j12 \Omega - j8\Omega} = \frac{120 \text{ A} \angle -180^\circ}{20 \angle -90^\circ} = 6 \text{ A} \angle -90^\circ \\ I_3 &= \frac{(8 \Omega \angle -90^\circ)(10 \text{ A} \angle -90^\circ)}{20 \Omega \angle -90^\circ} = \frac{80 \text{ A} \angle -180^\circ}{20 \angle -90^\circ} = 4 \text{ A} \angle -90^\circ \end{aligned}$$
- e.
$$V_L = (I \angle \theta)(X_L \angle 90^\circ) = (10 \text{ A} \angle -90^\circ)(6 \Omega \angle 90^\circ) = 60 \text{ V} \angle 0^\circ$$
3. a.
$$\begin{aligned} Z_T &= 4.7 \Omega \parallel (9.1 \Omega - j12 \Omega) = 4.7 \Omega \angle 0^\circ \parallel 15.06 \Omega \angle -52.826^\circ \\ &= \frac{70.782 \Omega \angle -52.826^\circ}{4.7 + 9.1 - j12} = \frac{70.782 \Omega \angle -52.826^\circ}{13.8 - j12} \\ &= \frac{70.782 \Omega \angle -52.826^\circ}{18.288 \angle -41.009^\circ} = 3.87 \Omega \angle -11.817^\circ \\ Y_T &= \frac{1}{Z_T} = \frac{1}{3.87 \Omega \angle -11.817^\circ} = 0.258 \text{ S} \angle 11.817^\circ \end{aligned}$$
- b.
$$I_s = \frac{E}{Z_T} = \frac{60 \text{ V} \angle 30^\circ}{3.87 \Omega \angle -11.817^\circ} = 15.504 \text{ A} \angle 41.871^\circ$$
- c. (CDR)
$$\begin{aligned} I_2 &= \frac{(4.7 \Omega \angle 0^\circ)(15.504 \text{ A} \angle 41.871^\circ)}{4.7 \Omega + 9.1 \Omega - j12 \Omega} = \frac{72.869 \text{ A} \angle 41.871^\circ}{18.288 \angle -41.009^\circ} \\ &= 3.985 \text{ A} \angle 82.826^\circ \end{aligned}$$
- d. (VDR)
$$\begin{aligned} V_C &= \frac{(12 \Omega \angle -90^\circ)(60 \text{ V} \angle 30^\circ)}{9.1 \Omega - j12 \Omega} = \frac{720 \text{ V} \angle -60^\circ}{15.06 \angle -52.826^\circ} \\ &= 47.809 \text{ V} \angle -7.174^\circ \end{aligned}$$
- e.
$$\begin{aligned} P &= EI \cos \theta = (60 \text{ V})(15.504 \text{ A})\cos(41.87^\circ - 30^\circ) \\ &= 930.24(0.979) = 910.71 \text{ W} \end{aligned}$$
5. a.
$$\begin{aligned} 400 \Omega \angle -90^\circ \parallel 400 \Omega \angle -90^\circ &= \frac{400 \Omega \angle -90^\circ}{2} = 200 \Omega \angle -90^\circ \\ Z' &= 200 \Omega - j200 \Omega = 282.843 \Omega \angle -45^\circ \\ Z'' &= 560 \Omega + j560 \Omega = 791.960 \Omega \angle 45^\circ \end{aligned}$$


$$\begin{aligned} Z_T = Z' \parallel Z'' &= \frac{(282.843 \angle -45^\circ)(791.960 \angle 45^\circ)}{(200 \angle -90^\circ - j200 \angle 0^\circ) + (560 \angle 0^\circ + j560 \angle 90^\circ)} \\ &= \frac{224,000.34 \angle 0^\circ}{840.952 \angle 25.346^\circ} = 266.365 \angle -25.346^\circ \end{aligned}$$

$$I = \frac{E}{Z_T} = \frac{100 \angle 0^\circ}{266.365 \angle -25.346^\circ} = 0.375 \angle 25.346^\circ$$

$$b. \quad V_C = \frac{(200 \angle -90^\circ)(100 \angle 0^\circ)}{200 \angle -90^\circ - j200 \angle 0^\circ} = \frac{20,000 \angle -90^\circ}{282.843 \angle -45^\circ} = 70.711 \angle -45^\circ$$

$$c. \quad P = EI \cos \theta = (100 \text{ V})(0.375 \text{ A}) \cos 25.346^\circ \\ = (37.5)(0.904) = 33.9 \text{ W}$$

7. a.

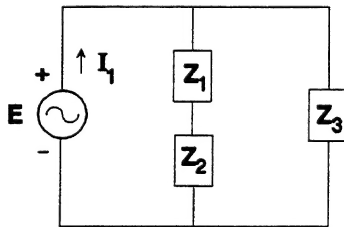

$$\begin{aligned} Z_1 &= 10 \angle 0^\circ \\ Z_2 &= 80 \angle 90^\circ \parallel 20 \angle 0^\circ \\ &= \frac{1600 \angle 90^\circ}{20 + j80} = \frac{1600 \angle 90^\circ}{82.462 \angle 75.964^\circ} \\ &= 19.403 \angle 14.036^\circ \\ Z_3 &= 60 \angle -90^\circ \end{aligned}$$


$$\begin{aligned} Z_T &= (Z_1 + Z_2) \parallel Z_3 \\ &= (10 \angle 0^\circ + 18.824 \angle 9.273^\circ + j4.706 \angle 90^\circ) \parallel 60 \angle -90^\circ \\ &= 29.206 \angle 9.273^\circ \parallel 60 \angle -90^\circ = \frac{1752.36 \angle -80.727^\circ}{28.824 + j4.706 - j60} \\ &= \frac{1752.36 \angle -80.727^\circ}{62.356 \angle -62.468^\circ} = 28.103 \angle -18.259^\circ \end{aligned}$$

$$I_1 = \frac{E}{Z_T} = \frac{40 \angle 0^\circ}{28.103 \angle -18.259^\circ} = 1.423 \angle 18.259^\circ$$

$$b. \quad V_1 = \frac{Z_2 E}{Z_2 + Z_1} = \frac{(19.403 \angle 14.036^\circ)(40 \angle 0^\circ)}{29.206 \angle 9.273^\circ} = \frac{776.12 \angle 14.036^\circ}{29.206 \angle 9.273^\circ} \\ = 26.574 \angle 4.763^\circ$$

$$c. \quad P = EI \cos \theta = (40 \text{ V})(1.423 \text{ A}) \cos 18.259^\circ \\ = 54.074 \text{ W}$$

9. a.

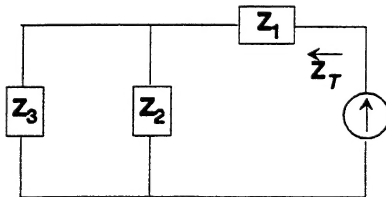

$$Z' = 3 \angle 0^\circ \parallel 4 \angle -90^\circ = \frac{12 \angle -90^\circ}{3 - j4}$$

$$= \frac{12 \angle -90^\circ}{5 \angle -53.13^\circ} = 2.4 \angle -36.87^\circ$$

$$\begin{aligned} Z_3 &= 2 Z' + j7 \angle 90^\circ \\ &= 4.8 \angle -36.87^\circ + j7 \angle 90^\circ \\ &= 3.84 \angle -90^\circ - j2.88 \angle 90^\circ + j7 \angle 90^\circ \\ &= 3.84 \angle -90^\circ + j4.12 \angle 90^\circ \\ &= 5.632 \angle 47.015^\circ \end{aligned}$$


$$\begin{aligned}
 Z_T &= Z_1 + Z_2 \parallel Z_3 = 6.8 \, \Omega + 8.2 \, \Omega \angle 0^\circ \parallel 5.632 \, \Omega \angle 47.015^\circ \\
 &= 6.8 \, \Omega + \frac{46.182 \, \Omega \angle 47.015^\circ}{8.2 + 3.84 + j4.12} = 6.8 \, \Omega + \frac{46.182 \, \Omega \angle 47.015^\circ}{12.725 \angle 18.891^\circ} \\
 &= 6.8 \, \Omega + 3.629 \, \Omega \angle 28.124^\circ = 6.8 \, \Omega + 3.201 \, \Omega + j1.711 \, \Omega \\
 &= 10 \, \Omega + j1.711 \, \Omega = 10.145 \, \Omega \angle 9.709^\circ
 \end{aligned}$$

$$Y_T = \frac{1}{Z_T} = 0.099 \, \text{S} \angle -9.709^\circ$$

b. $V_1 = IZ_1 = (3 \, \text{A} \angle 30^\circ)(6.8 \, \Omega \angle 0^\circ) = 20.4 \, \text{V} \angle 30^\circ$
 $V_2 = I(Z_2 \parallel Z_3) = (3 \, \text{A} \angle 30^\circ)(3.629 \, \Omega \angle 28.124^\circ)$
 $= 10.887 \, \text{V} \angle 58.124^\circ$

c. $I_3 = \frac{V_2}{Z_3} = \frac{10.877 \, \text{V} \angle 58.124^\circ}{5.632 \, \Omega \angle 47.015^\circ} = 1.933 \, \text{A} \angle 11.109^\circ$

11.

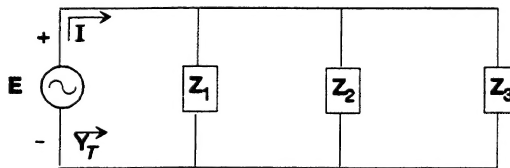

$$\begin{aligned}
 Z_1 &= 2 \, \Omega - j2 \, \Omega = 2.828 \, \Omega \angle -45^\circ \\
 Z_2 &= 3 \, \Omega - j9 \, \Omega + j6 \, \Omega \\
 &= 3 \, \Omega - j3 \, \Omega = 4.243 \, \Omega \angle -45^\circ \\
 Z_3 &= 10 \, \Omega \angle 0^\circ
 \end{aligned}$$

$$\begin{aligned}
 Y_T &= \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} = \frac{1}{2.828 \, \Omega \angle -45^\circ} + \frac{1}{4.243 \, \Omega \angle -45^\circ} + \frac{1}{10 \, \Omega \angle 0^\circ} \\
 &= 0.354 \, \text{S} \angle 45^\circ + 0.236 \, \text{S} \angle 45^\circ + 0.1 \, \text{S} \angle 0^\circ = 0.59 \, \text{S} \angle 45^\circ + 0.1 \, \text{S} \angle 0^\circ \\
 &= 0.417 \, \text{S} + j0.417 \, \text{S} + 0.1 \, \text{S} \\
 Y_T &= 0.517 \, \text{S} + j0.417 \, \text{S} = 0.664 \, \text{S} \angle 38.889^\circ \\
 Z_T &= \frac{1}{Y_T} = \frac{1}{0.664 \, \text{S} \angle 38.889^\circ} = 1.506 \, \Omega \angle -38.889^\circ \\
 I &= \frac{E}{Z_T} = \frac{50 \, \text{V} \angle 0^\circ}{1.506 \, \Omega \angle -38.889^\circ} = 33.201 \, \text{A} \angle 38.889^\circ
 \end{aligned}$$

13. $R_3 + R_4 = 2.7 \, \text{k}\Omega + 4.3 \, \text{k}\Omega = 7 \, \text{k}\Omega$
 $R' = 3 \, \text{k}\Omega \parallel 7 \, \text{k}\Omega = 2.1 \, \text{k}\Omega$
 $Z' = 2.1 \, \text{k}\Omega - j10 \, \Omega$

(CDR) $I' \text{ (of } 10 \, \Omega \text{ cap.)} = \frac{(40 \, \text{k}\Omega \angle 0^\circ)(20 \, \text{mA} \angle 0^\circ)}{40 \, \text{k}\Omega + 2.1 \, \text{k}\Omega - j10 \, \Omega}$
 $= 19 \, \text{mA} \angle +0.014^\circ$ as expected since $R_1 \gg Z'$

(CDR) $I_4 = \frac{(3 \, \text{k}\Omega \angle 0^\circ)(19 \, \text{mA} \angle 0.014^\circ)}{3 \, \text{k}\Omega + 7 \, \text{k}\Omega} = \frac{57 \, \text{mA} \angle 0.014^\circ}{10}$
 $= 5.7 \, \text{mA} \angle 0.014^\circ$
 $P = I^2 R = (5.7 \, \text{mA})^2 4.3 \, \text{k}\Omega = 139.71 \, \text{mW}$

CHAPTER 16 (Even)

2. a.
$$\begin{aligned} Z_T &= 3 \Omega + j6 \Omega + 2 \Omega \angle 0^\circ \parallel 8 \Omega \angle -90^\circ \\ &= 3 \Omega + j6 \Omega + 1.94 \Omega \angle -14.04^\circ \\ &= 3 \Omega + j6 \Omega + 1.882 \Omega - j0.471 \Omega \\ &= 4.882 \Omega + j5.529 \Omega = 7.376 \Omega \angle 48.556^\circ \end{aligned}$$
- b.
$$I_s = \frac{E}{Z_T} = \frac{30 \text{ V} \angle 0^\circ}{7.376 \Omega \angle 48.556^\circ} = 4.067 \text{ A} \angle -48.556^\circ$$
- c.
$$\begin{aligned} I_C &= \frac{Z_{R_2} I_s}{Z_{R_2} + Z_C} = \frac{(2 \Omega \angle 0^\circ)(4.067 \text{ A} \angle -48.556^\circ)}{2 \Omega - j8 \Omega} \\ &= \frac{8.134 \text{ A} \angle -48.556^\circ}{8.246 \angle -75.964^\circ} = 0.986 \text{ A} \angle 27.408^\circ \end{aligned}$$
- d.
$$\begin{aligned} V_L &= \frac{Z_L E}{Z_T} = \frac{(6 \Omega \angle 90^\circ)(30 \text{ V} \angle 0^\circ)}{7.376 \Omega \angle 48.556^\circ} = \frac{180 \text{ V} \angle 90^\circ}{7.376 \angle 48.556^\circ} \\ &= 24.403 \text{ V} \angle 41.44^\circ \end{aligned}$$
4. a.
$$\begin{aligned} Z_T &= 2 \Omega + \frac{(4 \Omega \angle -90^\circ)(6 \Omega \angle 90^\circ)}{-j4 \Omega + j6 \Omega} + \frac{4 \Omega \angle 0^\circ(3 \Omega \angle 90^\circ)}{4 \Omega + j3 \Omega} \\ &= 2 \Omega + \frac{24 \Omega \angle 0^\circ}{2 \angle 90^\circ} + \frac{12 \Omega \angle 90^\circ}{5 \angle 36.87^\circ} \\ &= 2 \Omega + 12 \Omega \angle -90^\circ + 2.4 \angle 53.13^\circ \\ &= 2 \Omega - j12 \Omega + 1.44 \Omega + j1.92 \Omega \\ &= 3.44 \Omega - j10.08 \Omega = 10.65 \Omega \angle -71.16^\circ \end{aligned}$$
- b.
$$\begin{aligned} V_2 &= I(2.4 \Omega \angle 53.13^\circ) = (5 \text{ A} \angle 0^\circ)(2.4 \Omega \angle 53.13^\circ) = 12 \text{ V} \angle 53.13^\circ \\ I_L &= \frac{(4 \Omega \angle 0^\circ)(I)}{4 \Omega + j3 \Omega} = \frac{(4 \Omega \angle 0^\circ)(5 \text{ A} \angle 0^\circ)}{5 \Omega \angle 36.87^\circ} = \frac{20 \text{ A} \angle 0^\circ}{5 \angle 36.87^\circ} = 4 \text{ A} \angle -36.87^\circ \end{aligned}$$
- c.
$$F_p = \frac{R}{Z_T} = \frac{3.44 \Omega}{10.65 \Omega} = 0.323 \text{ (leading)}$$
6. a.
$$\begin{aligned} Z_1 &= 3 \Omega + j4 \Omega = 5 \Omega \angle 53.13^\circ \\ I_1 &= \frac{E}{Z_1} = \frac{120 \text{ V} \angle 60^\circ}{5 \Omega \angle 53.13^\circ} = 24 \text{ A} \angle 6.87^\circ \end{aligned}$$
- b.
$$V_C = \frac{(13 \Omega \angle -90^\circ)(120 \text{ V} \angle 60^\circ)}{-j13 \Omega + j7 \Omega} = \frac{1560 \text{ V} \angle -30^\circ}{6 \angle -90^\circ} = 260 \text{ V} \angle 60^\circ$$
- c.
$$\begin{aligned} V_{R_1} &= (I_1 \angle \theta)R \angle 0^\circ = (24 \text{ A} \angle 6.87^\circ)(3 \Omega \angle 0^\circ) = 72 \text{ V} \angle 6.87^\circ \\ V_{ab} + V_{R_1} - V_C &= 0 \\ V_{ab} &= V_C - V_{R_1} = 260 \text{ V} \angle 60^\circ - 72 \text{ V} \angle 6.87^\circ \\ &= (130 \text{ V} + j225.167 \text{ V}) - (71.483 \text{ V} + j8.612 \text{ V}) \\ &= 58.517 \text{ V} + j216.555 \text{ V} = 224.32 \text{ V} \angle 74.88^\circ \end{aligned}$$

8. a. $Z_1 = 2 \Omega + j1 \Omega = 2.236 \Omega \angle 26.565^\circ$, $Z_2 = 3 \Omega \angle 0^\circ$
 $Z_3 = 16 \Omega + j15 \Omega - j7 \Omega = 16 \Omega + j8 \Omega = 17.889 \Omega \angle 26.565^\circ$
 $Y_T = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} = \frac{1}{2.236 \Omega \angle 26.565^\circ} + \frac{1}{3 \Omega \angle 0^\circ} + \frac{1}{17.889 \Omega \angle 26.565^\circ}$
 $= 0.447 \text{ S} \angle -26.565^\circ + 0.333 \text{ S} \angle 0^\circ + 0.056 \text{ S} \angle -26.565^\circ$
 $= (0.4 \text{ S} - j0.2 \text{ S}) + (0.333 \text{ S}) + (0.05 \text{ S} - j0.025 \text{ S})$
 $= 0.783 \text{ S} - j0.225 \text{ S} = 0.815 \text{ S} \angle -16.032^\circ$
 $Z_T = \frac{1}{Y_T} = \frac{1}{0.815 \text{ S} \angle -16.032^\circ} = 1.227 \Omega \angle 16.032^\circ$
- b. $I_1 = \frac{E}{Z_1} = \frac{60 \text{ V} \angle 0^\circ}{2.236 \Omega \angle 26.565^\circ} = 26.834 \text{ A} \angle -26.565^\circ$
 $I_2 = \frac{E}{Z_2} = \frac{60 \text{ V} \angle 0^\circ}{3 \Omega \angle 0^\circ} = 20 \text{ A} \angle 0^\circ$
 $I_3 = \frac{E}{Z_3} = \frac{60 \text{ V} \angle 0^\circ}{17.889 \Omega \angle 26.565^\circ} = 3.354 \text{ A} \angle -26.565^\circ$
- c. $I_s = \frac{E}{Z_T} = \frac{60 \text{ V} \angle 0^\circ}{1.227 \Omega \angle 16.032^\circ} = 48.9 \text{ A} \angle -16.032^\circ$
 $I_s \stackrel{?}{=} I_1 + I_2 + I_3$
 $48.9 \text{ A} \angle -16.032^\circ \stackrel{?}{=} 26.834 \text{ A} \angle -26.565^\circ + 20 \text{ A} \angle 0^\circ + 3.354 \text{ A} \angle -26.565^\circ$
 $= (24 \text{ A} - j12 \text{ A}) + (20 \text{ A}) + (3 \text{ A} - j1.5 \text{ A})$
 $\checkmark = 47 \text{ A} + j13.5 \text{ A} = 48.9 \text{ A} \angle -16.026^\circ \text{ (checks)}$
- d. $F_p = \frac{G}{Y_T} = \frac{0.783 \text{ A}}{0.815 \text{ S}} = 0.961 \text{ (lagging)}$
10. a. $X_{L_1} = \omega L_1 = 2\pi(10^3 \text{ Hz})(0.1 \text{ H}) = 628 \Omega$
 $X_{L_2} = \omega L_2 = 2\pi(10^3 \text{ Hz})(0.2 \text{ H}) = 1.256 \text{ k}\Omega$
 $X_C = \frac{1}{\omega C} = \frac{1}{2\pi(10^3 \text{ Hz})(1 \mu\text{F})} = 0.159 \text{ k}\Omega$
 $Z_T = R \angle 0^\circ + X_{L_1} \angle 90^\circ + X_C \angle -90^\circ \parallel X_{L_2} \angle 90^\circ$
 $= 300 \Omega + j628 \Omega + 0.159 \text{ k}\Omega \angle -90^\circ \parallel 1.256 \text{ k}\Omega \angle 90^\circ$
 $= 300 \Omega + j628 \Omega - j182 \Omega$
 $= 300 \Omega + j446 \Omega = 537.51 \Omega \angle 56.07^\circ$
 $Y_T = \frac{1}{Z_T} = \frac{1}{537.51 \Omega \angle 56.07^\circ} = 1.86 \text{ mS} \angle -56.07^\circ$
- b. $I_s = \frac{E}{Z_T} = \frac{50 \text{ V} \angle 0^\circ}{537.51 \Omega \angle 56.07^\circ} = 93 \text{ mA} \angle -56.07^\circ$

$$\begin{aligned}
 \text{c. (CDR): } I_1 &= \frac{Z_{L_2} I_s}{Z_{L_2} + Z_C} = \frac{(1.256 \text{ k}\Omega \angle 90^\circ)(93 \text{ mA} \angle -56.07^\circ)}{+j1.256 \text{ k}\Omega - j0.159 \text{ k}\Omega} \\
 &= \frac{116.81 \text{ mA} \angle 33.93^\circ}{1.097 \angle 90^\circ} = 106.48 \text{ mA} \angle -56.07^\circ \\
 I_2 &= \frac{Z_C I_s}{Z_{L_2} + Z_C} = \frac{(0.159 \text{ k}\Omega \angle -90^\circ)(93 \text{ mA} \angle -56.07^\circ)}{1.097 \text{ k}\Omega \angle 90^\circ} \\
 &= \frac{14.79 \text{ mA} \angle -146.07^\circ}{1.097 \angle 90^\circ} = 13.48 \text{ mA} \angle -236.07^\circ \\
 &= 13.48 \text{ mA} \angle 123.93^\circ
 \end{aligned}$$

$$\begin{aligned}
 \text{d. } V_1 &= (I_2 \angle \theta)(X_{L_2} \angle 90^\circ) = (13.48 \text{ mA} \angle 123.92^\circ)(1.256 \text{ k}\Omega \angle 90^\circ) \\
 &= 16.931 \text{ V} \angle 213.93^\circ \\
 V_{ab} &= E - (I_s \angle \theta)(R \angle 0^\circ) = 50 \text{ V} \angle 0^\circ - (93 \text{ mA} \angle -56.07^\circ)(300 \Omega \angle 0^\circ) \\
 &= 50 \text{ V} - 27.9 \text{ V} \angle -56.07^\circ \\
 &= 50 \text{ V} - (15.573 \text{ V} - j23.149 \text{ V}) \\
 &= 34.43 \text{ V} + j23.149 \text{ V} = 41.49 \text{ V} \angle 33.92^\circ
 \end{aligned}$$

$$\text{e. } P = I_s^2 R = (93 \text{ mA})^2 300 \Omega = 2.595 \text{ W}$$

$$\text{f. } F_p = \frac{R}{Z_T} = \frac{300 \Omega}{537.51 \Omega} = 0.558 \text{ (lagging)}$$

$$\begin{aligned}
 12. \quad Z' &= 12 \Omega - j20 \Omega = 23.324 \Omega \angle -59.036^\circ \\
 R_4 \angle 0^\circ \parallel Z' &= 20 \Omega \angle 0^\circ \parallel 23.324 \Omega \angle -59.036^\circ = 12.362 \Omega \angle -27.031^\circ \\
 Z'' &= R_3 \angle 0^\circ + R_4 \angle 0^\circ \parallel Z' = 12 \Omega + 12.362 \Omega \angle -27.031^\circ \\
 &= 12 \Omega + (11.012 \Omega - j5.618 \Omega) \\
 &= 23.012 \Omega - j5.618 \Omega = 23.688 \Omega \angle -13.719^\circ \\
 R_2 \angle 0^\circ \parallel Z'' &= 20 \Omega \angle 0^\circ \parallel 23.688 \Omega \angle -13.719^\circ = 10.922 \Omega \angle -6.277^\circ \\
 Z_T &= R_1 \angle 0^\circ + R_2 \angle 0^\circ \parallel Z'' = 12 \Omega + 10.922 \Omega \angle -6.277^\circ \\
 &= 12 \Omega + (10.857 \Omega - j1.194 \Omega) \\
 &= 22.857 \Omega - j1.194 \Omega = 22.888 \Omega \angle -2.99^\circ
 \end{aligned}$$

$$I_s = \frac{E}{Z_T} = \frac{100 \text{ V} \angle 0^\circ}{22.888 \Omega \angle -2.99^\circ} = 4.371 \text{ A} \angle 2.99^\circ$$

$$I_{R_1} = I$$

$$\begin{aligned}
 I_{R_3} &= \frac{R_2 \angle 0^\circ I_s}{R_2 \angle 0^\circ + Z''} = \frac{(20 \Omega \angle 0^\circ)(4.371 \text{ A} \angle 2.99^\circ)}{\underbrace{20 \Omega + 23.012 \Omega - j5.618 \Omega}_{43.012 \Omega}} = \frac{87.42 \text{ A} \angle 2.99^\circ}{43.377 \angle -7.442^\circ} \\
 &= 2.015 \text{ A} \angle 10.432^\circ
 \end{aligned}$$

$$\begin{aligned}
 I_5 &= \frac{R_4 \angle 0^\circ I_{R_3}}{R_4 \angle 0^\circ + Z'} = \frac{(20 \Omega \angle 0^\circ)(2.015 \text{ A} \angle 10.432^\circ)}{\underbrace{20 \Omega + 12 \Omega - j20 \Omega}_{32 \Omega}} = \frac{40.3 \text{ A} \angle 10.432^\circ}{37.736 \angle -32.005^\circ} \\
 &= 1.068 \text{ A} \angle 42.437^\circ
 \end{aligned}$$

$$14. \quad \mathbf{Z}' = X_{C_2} \angle -90^\circ \parallel R_1 \angle 0^\circ = 2 \, \Omega \angle -90^\circ \parallel 1 \, \Omega \angle 0^\circ$$

$$= \frac{2 \, \Omega \angle -90^\circ}{1 - j2} = \frac{2 \, \Omega \angle -90^\circ}{2.236 \angle -63.435^\circ}$$

$$= 0.894 \, \Omega \angle -26.565^\circ$$

$$\mathbf{Z}'' = X_{L_2} \angle 90^\circ + \mathbf{Z}' = +j8 \, \Omega + 0.894 \, \Omega \angle -26.565^\circ$$

$$= +j8 \, \Omega + (0.8 \, \Omega - j4 \, \Omega)$$

$$= 0.8 \, \Omega + j4 = 4.079 \, \Omega \angle 78.69^\circ$$

$$\mathbf{I}_{X_{L_2}} = \frac{X_{C_1} \angle -90^\circ \mathbf{I}}{X_{C_1} \angle -90^\circ + \mathbf{Z}''} = \frac{2 \, \Omega (\angle -90^\circ)(0.5 \, \text{A} \angle 0^\circ)}{-j2 \, \Omega + (0.8 \, \Omega + j4 \, \Omega)} = \frac{1 \, \text{A} \angle -90^\circ}{0.8 + j2}$$

$$= \frac{1 \, \text{A} \angle -90^\circ}{2.154 \angle 68.199^\circ} = 0.464 \, \text{A} \angle -158.99^\circ$$

$$\mathbf{I}_1 = \frac{X_{C_2} \angle -90^\circ \mathbf{I}_{X_{L_2}}}{X_{C_2} \angle -90^\circ + R_1} = \frac{(2 \, \Omega \angle -90^\circ)(0.464 \, \text{A} \angle -158.99^\circ)}{-j2 \, \Omega + 1 \, \Omega} = \frac{0.928 \, \text{A} \angle -248.99^\circ}{2.236 \angle -63.435^\circ}$$

$$= 0.415 \, \text{A} \angle 174.45^\circ$$